 


NAME: ANANYA PRASAD  
 REG NO: 20BCE10093  
 SUBJECT: ECE2002  
 SLOT: B11+B12+B13  
 FACULTY: DR JITENDRA KUMAR

### ASSIGNMENT-3

- 1 Write the function of half adder. Draw and explain various implementations.  
 A combinational circuit that performs the addition of two bits is called a half adder. There are two input bits and the output consists of sum and carry bits.




TRUTH TABLE  $\Rightarrow$

A	B	S	C
0	0	0	0
0	1	1	0
1	1	1	0
1	0	0	1


To find the SUM, we have XOR gate  $\Rightarrow \text{SUM} = A \text{ XOR } B = A \oplus B$

To find the carry, we have AND gate  $\Rightarrow \text{CARRY} = A \text{ AND } B = AB$

LOGIC GATE

 

LOGIC GATE WITHOUT USING XOR GATE

 

$$S = AB' + A'B$$


$$C = AB$$

TRUTH TABLE

A	B	S	C
0	0	0	0
0	1	1	0
1	1	1	0
1	0	0	1
 
## 2 Explain half subtractor.

Half subtractor is a building block for subtracting two binary numbers. It has two inputs and two outputs. The inputs are two single bit binary numbers and the output are difference and borrow.




Boolean expression  $\Rightarrow$  EXOR for difference  
NAND for borrow

### TRUTH TABLE

A	B	D	B <sub>0</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

### LOGIC GATE

 

## 3 What is the function of binary multiplier? Explain

A binary multiplier is used to multiply two binary numbers. The two numbers are specifically known as multiplicand and multiplier and the result is known as product.

The bit size of the product is equal to the sum of the bit size of multiplier and multiplicand.


For 1 bit  $\rightarrow$  same as ~~binary~~ decimal multiplication

### 2x2 Bit multiplier
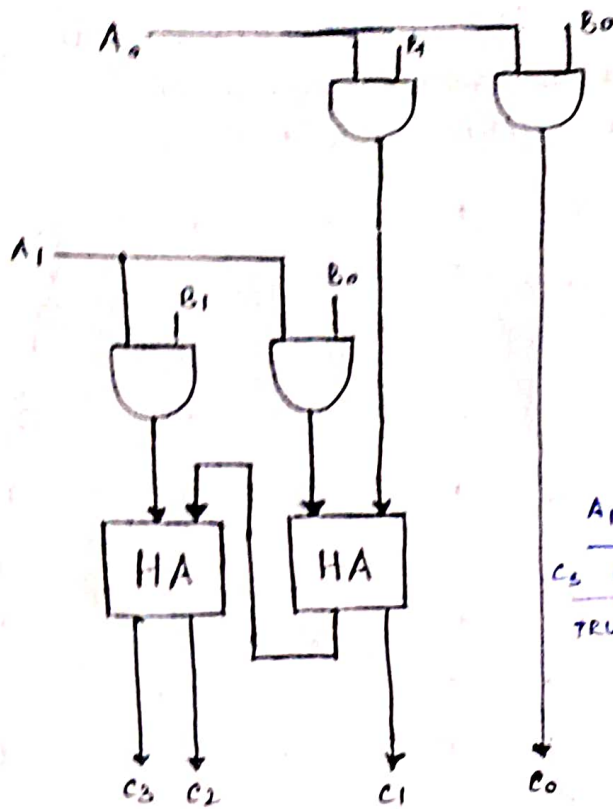
#### 2-bit Full adder

The partial product of LSBs of inputs is the LSB of product.


The other terms of each partial product should be considered and added using a 2-bit full adder.



$B_1$	$B_0$
$A_1$	$A_0$
<hr/>	
$A_0 B_1$	$A_0 B_0$
$A_1 B_1$	$A_1 B_0$
$C_3$	$C_2$
$C_1$	$C_0$

TRUTH TABLE		MULTIPLIER BITS		MULTIPLICAND	
$i+1$	$y_1$	MULTIPLES		IMP.	
0	0	0		0	
0	1	1		x	
1	0	2		Shift left x	
1	1	3		Shift left x + x	

4x3 bit Multiplier

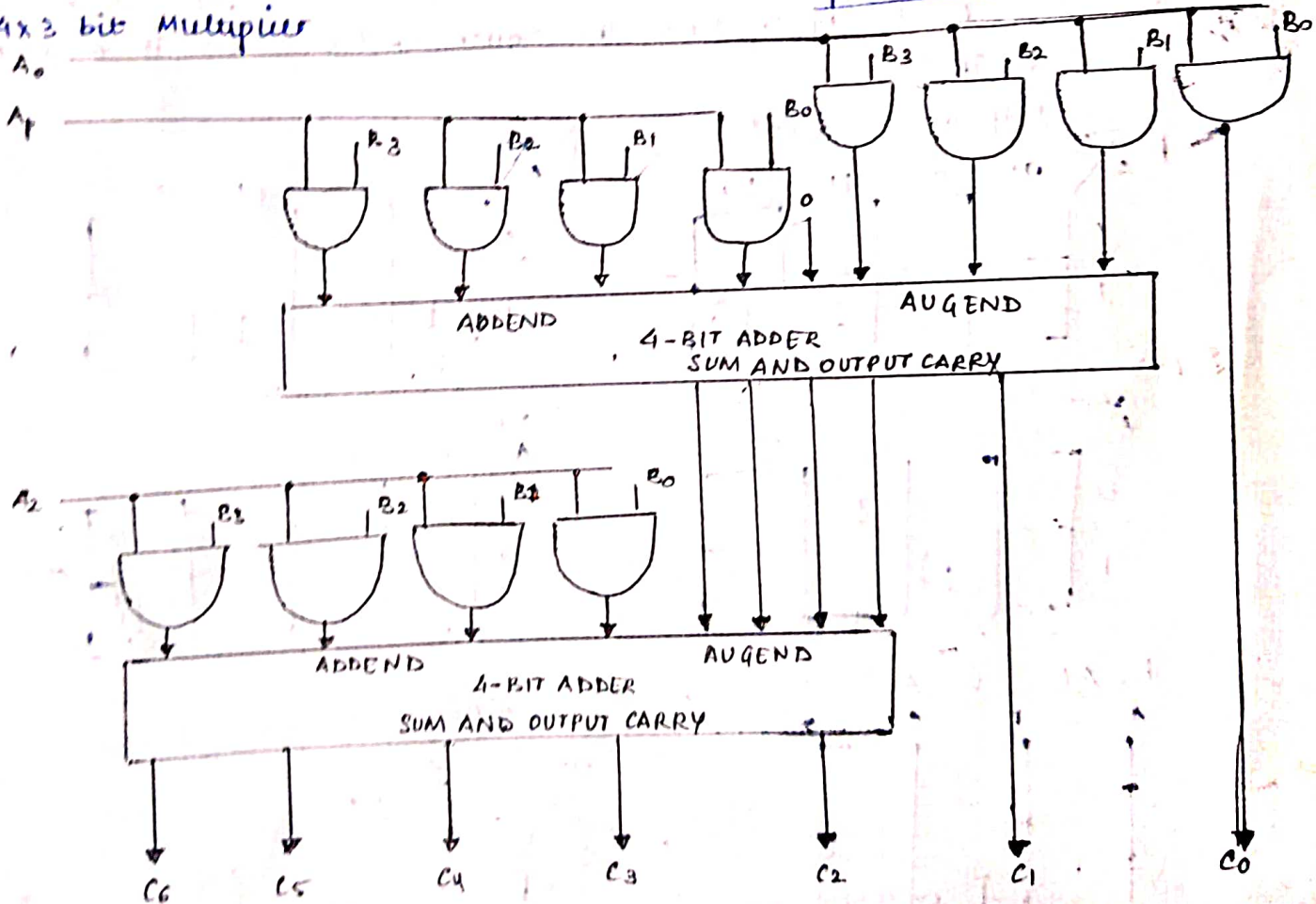



Design a computational circuit that accepts a 3-bit number and generates an output binary number equal to the square of input number.  
A 3-bit register has  $2^3$  possible combination of inputs.

A	B	C	P	Q	R	S	T	U
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0	1

Truth table, we have 3bits input and 6 outputs on the left side. We have total of 8 possible inputs since the square of 8 is 64, so it needs maximum of 6 bits spaces.

For K-Map for P, Q, R and S.

P  $\Rightarrow$  BC

A \ BC	00	01	11	10
0				
1			1	1

Q  $\Rightarrow$  BC

A \ BC	00	01	11	10
0				
1	1	1	1	


R  $\Rightarrow$  BC

A \ BC	00	01	11	10
0			1	
1		1		

S  $\Rightarrow$  BC

A \ BC	00	01	11	10
0				1
1				1

 
$$P = AB ; Q = AB' + AC ; R = AB'C + A'BC / C(A \oplus B) ; S = BC'$$



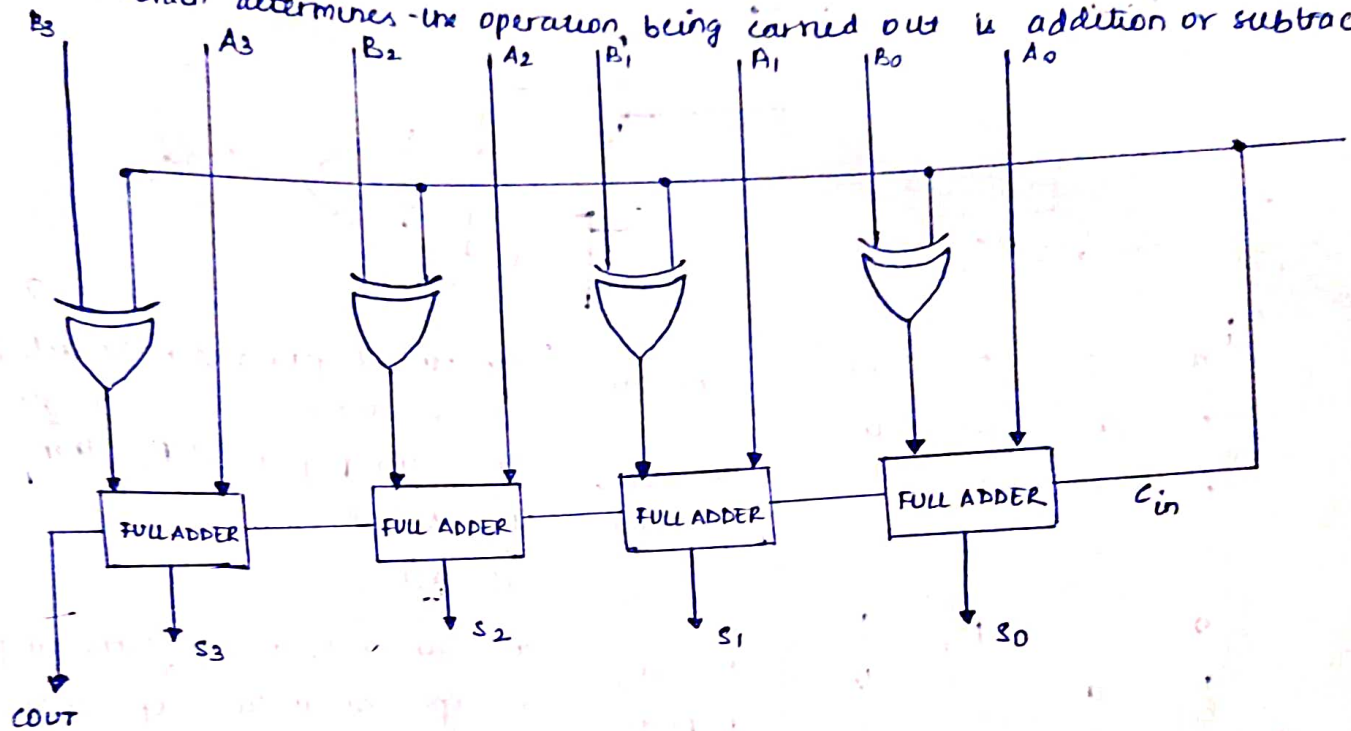5. Design a 4-bit adder subtractor circuit and explain operation in details. Let us consider two 4-bit binary numbers A and B as inputs to the digital circuit for the operation with digits.

$A_0, A_1, A_2, A_3$  for A  
 $B_0, B_1, B_2, B_3$  for B

The circuit consists of 4 full adders since we are performing operation on 4-bit numbers. There is a control line K that holds a binary value of either 0 or 1 which determines the operation being carried out is addition or subtraction.



As shown, the first full adder has control line directly as its input (input carry  $C_0$ ). The input  $A_0$  (The least significant bit of A) is directly input in the full adder. The third input is the EXOR of  $B_0$  and K (S in fig, but do not confuse it with sum-S). The two outputs produced are the sum/difference ( $S_0$ ) and carry ( $C_1$ ). If the value of K (control line) is 1, Output of  $B_0$  (EXOR)  $K = B_0'$  (complement  $B_0$ ). Thus the operation would be  $A + B_0'$ . Now 2's complement subtraction for two numbers A and B is given by  $A + B'$ . This suggests that when  $K=1$ , the operation being performed on the four bit numbers is subtraction. Similarly, if the value of  $K=0$ ,  $B_0$  (EXOR)  $K = B_0$ . The operation is  $A + B$  which is simple binary addition. This suggests that when  $K=0$ , the operation being performed on the four bit numbers is addition.


Then  $C_0$  is serially passed to the second full adder as one of its inputs. The sum/difference  $S_0$  is recorded as the least significant bit of the sum/diff.  $A_1, A_2, A_3$  are direct inputs to the second, third and fourth full adders. Then carry  $C_1, C_2$  are serially passed to the successive full adder as one of the inputs.  $C_3$  becomes the total carry to the sum/difference.  $S_1, S_2$  and  $S_3$  are recorded to form the result with  $S_0$ .



6

Draw and explain the working of carry look ahead adder.

 A carry look ahead adder reduces the propagation delay by introducing more complex hardware. In this design, the ripple carry design is suitably transformed such that the carry logic over fixed groups of bits of the adder is reduced to two-level logic.



A	B	C	C+1	Condition
0	0	0	0	No carry Generate
0	0	1	0	
0	1	0	0	
0	1	1	1	No Carry Propagate
1	0	0	0	
1	0	1	1	
1	1	0	1	Carry Generate
1	1	1	1	

Consider the full adder circuit shown has two variables as 'carry generate'  $G_i$  and 'carry propagate'  $P_i$ , then,

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

The sum output and carry output can be expressed in terms of carry generate  $G_i$  and carry propagate  $P_i$  as.

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

where  $G_i$  produces the carry when both

$A_i B_i$  are 1 regardless of the input carry.  $P_i$  is associated with the propagation of carry from  $C_i$  to  $C_{i+1}$ .

The carry output Boolean function of each stage in a 4 stage carry look ahead adder can be expressed as

$$C_1 = G_0 + P_0 C_{in}$$


$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_{in}$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{in}$$


$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{in}$$

From the above Boolean equations we can observe that  $C_4$  does not have to wait for  $C_3$  and  $C_2$  to propagate but  $C_4$  is propagated at the same time as  $C_3$  and  $C_2$ . Since the Boolean expression for each carry output is the sum of products so these can be implemented with one level of AND gates followed by an OR gate.

 7 Explain the functionality of a decoder  
 It is a combinational circuit that converts  $n$  lines of input into  $2^n$  lines of output.  
 At a time, only one input line is activated for simplicity. The produced  $2^n$ -bit output code is equivalent to the binary information.



 There are various types of decoders, to demonstrate, let's discuss 2 to 4 line decoder. There are three inputs  $A_0$ ,  $A_1$ , and  $E$  and four outputs  $Y_0$ ,  $Y_1$ ,  $Y_2$ ,  $Y_3$ . For each combination of inputs, when the enable  $E$  is set to 1, one of these four outputs will be 1. The block diagram and the truth table of 2 to 4 line decoder →



ENABLE	INPUTS		OUTPUTS			
	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
$E$	$X$	$X$	0	0	0	0
0	0	0	0	0	0	1
1	0	1	0	0	1	0
1	0	1	0	1	0	0
1	1	0	1	0	0	0
1	1	1	0	0	0	0

The logical expression of the term  $Y_0$ ,  $Y_1$ ,  $Y_2$  and  $Y_3$  are as follows:


$$Y_3 = E \cdot A_1 \cdot A_0$$

$$Y_2 = E \cdot A_1 \cdot A_0'$$

$$Y_1 = E \cdot A_1' \cdot A_0$$

$$Y_0 = E \cdot A_1' \cdot A_0'$$

Logical circuit.

 




8 With a neat diagram explain 3-8 decoder.

The 3-8 line decoder is also called Binary to Octal decoder. There are a total of eight outputs, i.e.,  $Y_0, Y_1, Y_2, Y_3, Y_4, Y_5, Y_6, Y_7$  and three inputs  $A_0, A_1, A_2$ .

 This circuit has an enable  $E$ . When the enable ' $E$ ' is set to 1. The block diagram and Truth table  $\Rightarrow$



Logical expressions  $\Rightarrow$

$$Y_0 = A_0' \cdot A_1' \cdot A_2'$$

$$Y_1 = A_0 \cdot A_1' \cdot A_2'$$

$$Y_2 = A_0' \cdot A_1 \cdot A_2'$$

$$Y_3 = A_0 \cdot A_1 \cdot A_2'$$

$$Y_4 = A_0' \cdot A_1' \cdot A_2$$

$$Y_5 = A_0 \cdot A_1' \cdot A_2$$


$$Y_6 = A_0' \cdot A_1 \cdot A_2$$

$$Y_7 = A_0 \cdot A_1 \cdot A_2$$

TRUTH TABLE :

ENABLE		INPUTS			OUTPUTS							
$E$		$A_0$	$A_1$	$A_2$	$Y_7$	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0		X	X	X	0	0	0	0	0	0	0	0
1		0	0	0	0	0	0	0	0	0	1	0
1		0	0	1	0	0	0	0	0	1	0	0
1		0	1	0	0	0	0	0	1	0	0	0
1		0	1	1	0	0	0	1	0	0	0	0
1		1	0	0	0	0	0	1	0	0	0	0
1		1	0	1	0	0	1	0	0	0	0	0
1		1	1	0	0	1	0	0	0	0	0	0
1		1	1	1	1	0	0	0	0	0	0	0




 

9 Implement using a 8:1 MUX

(2)  $F(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15)$

	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
$\bar{A}$	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	1	0	$\bar{A}$	$\bar{A}$	0	0	A

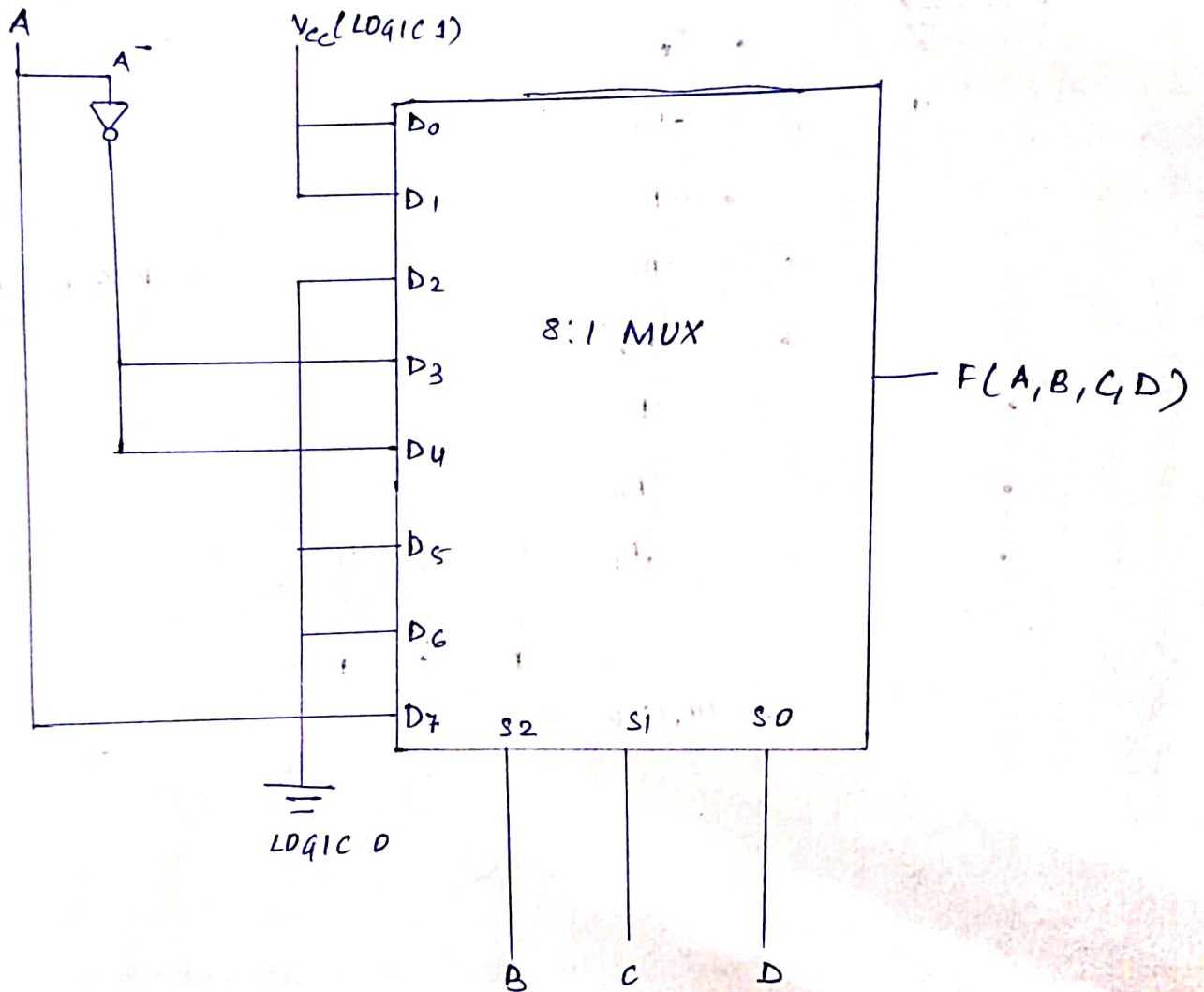




(u)

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$

	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
$\bar{A}$	0	(1)	2	(3)	(4)	5	6	7
A	8	9	10	(11)	(12)	(13)	(14)	(15)
	0	$\bar{A}$	0	1	1	A	A	A

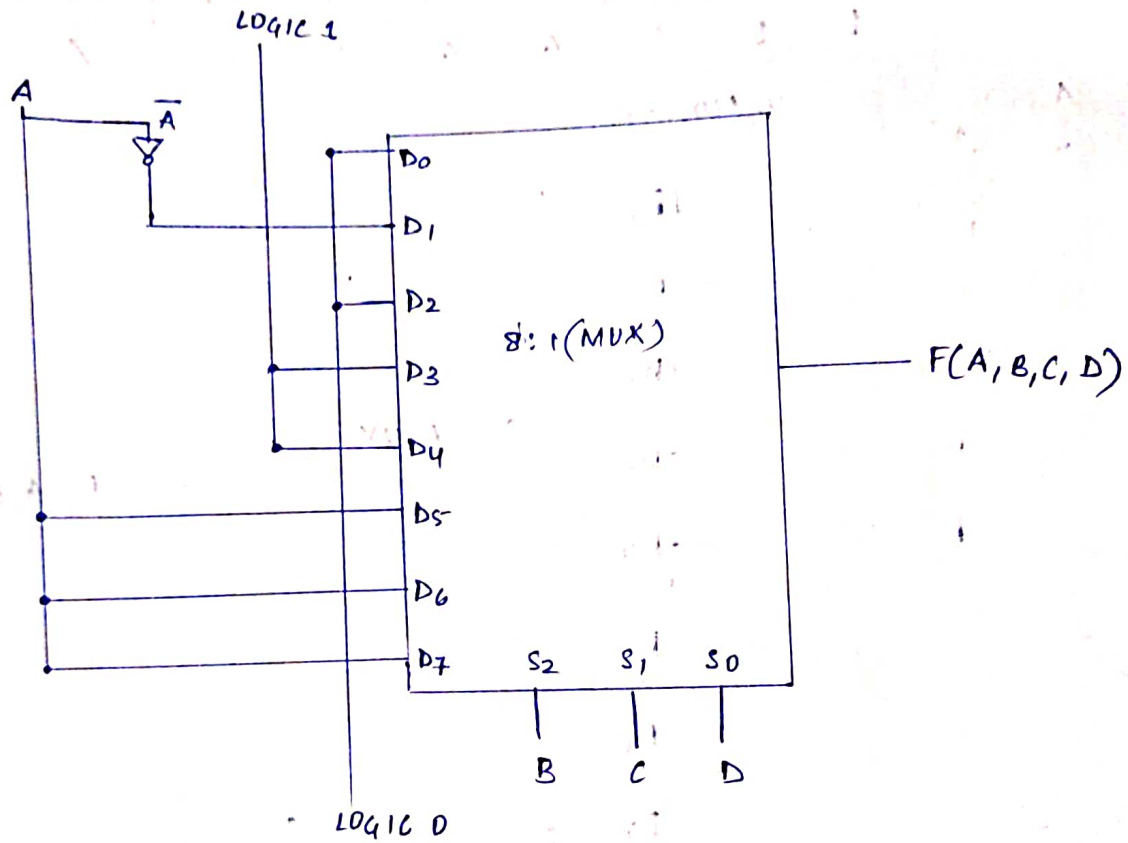


The basic Flipflop circuit with NAND GATE is SR FLIPFLOP.

This simple flipflop is basically a one-bit memory bistable device that has two inputs one which will 'SET' the device (labelled S) and the other which 'reset' the device (labelled R)

SR stands for 'set-reset'. The reset input resets the flipflop back to its original state with an output Q that will be either at a logic level '1' or logic "0" depending upon set/reset condition

 The simplest way to make an SR Flipflop, just connect together a pair of cross coupled 2-input NAND gates, to form a set/reset bistable also known as an active LOW SR NAND gate latch, so there is feedback from each output to one of the other NAND gate inputs. The device has two inputs, one is set (S), other reset (R) and corresponding outputs Q and its complement  $\bar{Q}$ .



TRUTH TABLE

	S	R	Q		
Set	1	0	0	1	Set $\bar{Q} > 1$
	1	1	0	1	No change
Reset	0	1	1	0	Reset $\bar{Q} > 0$
	1	1	1	0	no change
Invalid	0	0	1	1	Invalid