

Name: Ananya Prasad


Reg No: 20BCE10093

Sect: EEE1001/E11


Faculty: Soumitra Sir

Date: / /  
Page No.

30/9/21

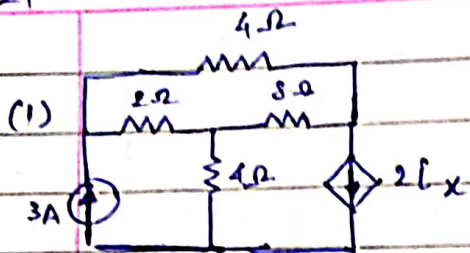

→

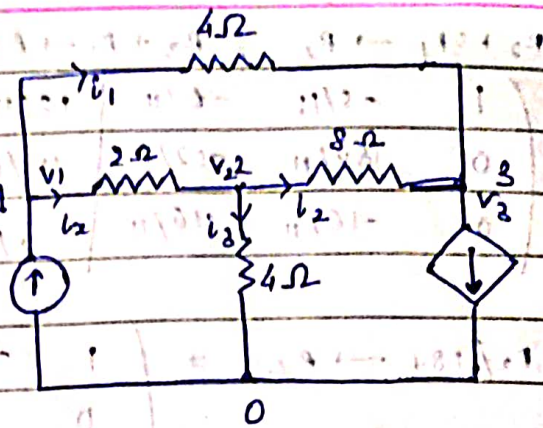

3 nodes

KCL at node 1  $\Rightarrow 3 = 0 + i_x$

$$= 3 = \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2}$$

$$= 3v_1 - 2v_2 - v_3 = 12 \quad \rightarrow (1)$$

KCL at node 2  $\Rightarrow$

$$i_x = i_1 + i_3 \Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{8} + \frac{v_2 - 0}{4}$$

$$= -4v_1 + 7v_2 - v_3 = 0 \quad \rightarrow (2)$$


KCL at node 3  $\Rightarrow$

$$i_1 + i_2 = 2i_x$$

$$\Rightarrow \frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = 2 \frac{v_1 - v_2}{2} \Rightarrow 2v_1 - 3v_2 + v_3 = 0 \quad \rightarrow (3)$$

From (1), (2) and (3),
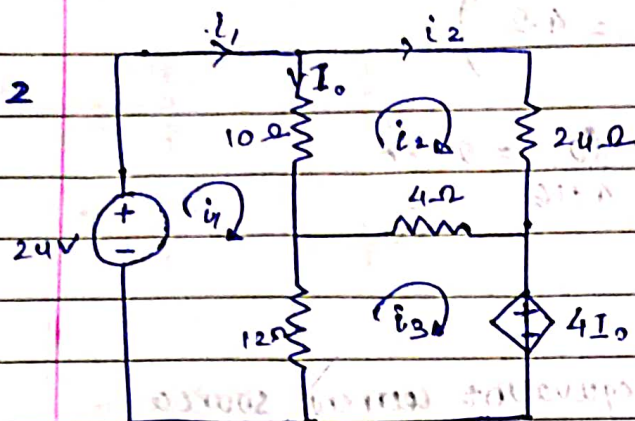
$$v_1 = \frac{24}{5} \text{ V} ; v_2 = \frac{12}{5} \text{ V} ; v_3 = -\frac{12}{5} \text{ V}$$



In Mesh 1, KVL

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$

$$11i_1 - 5i_2 - 6i_3 = 12$$

In mesh 2, KVL

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$-5i_1 + 19i_2 - 2i_3 = 0$$

$$\text{In mesh 3, } 4I_0 + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$\text{at } I_0 = i_1 - i_2,$$

$$4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$-i_1 - i_2 + 2i_3 = 0$$

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

by crammer's rule ;

$$\left( \begin{array}{ccc|c} 11 & -5 & -6 & 12 \\ -5 & 19 & -2 & 0 \\ -1 & -1 & 2 & 0 \end{array} \right)$$

 $R_1/11 \rightarrow R_1$ 

$$\left( \begin{array}{ccc|c} 1 & -5/11 & -6/11 & 12/11 \\ -5 & 19 & -2 & 0 \\ -1 & -1 & 2 & 0 \end{array} \right)$$



$$R_2 + 5R_1 \rightarrow R_2 ; R_3 + R_1 \rightarrow R_3$$

$$\left( \begin{array}{ccc|c} 1 & -5/11 & -6/11 & 12/11 \\ 0 & 184/11 & -52/11 & 15/46 \\ 0 & -16/11 & 16/11 & 12/11 \end{array} \right)$$

$$R_2 / 184 \rightarrow R_2$$

$$\Rightarrow \left( \begin{array}{ccc|c} 1 & -5/11 & -6/11 & 12/11 \\ 0 & 1 & -13/46 & 15/46 \\ 0 & -16/11 & 16/11 & 12/11 \end{array} \right)$$

$$R_1 + 5R_2 \rightarrow R_1 ; R_3 + 16R_2 \rightarrow R_3$$

$$\left( \begin{array}{ccc|c} 1 & 0 & -31/46 & 57/46 \\ 0 & 1 & -13/46 & 15/46 \\ 0 & 0 & 24/23 & 36/23 \end{array} \right)$$

$$R_3 / \frac{24}{23} \rightarrow R_3$$

$$\Rightarrow \left( \begin{array}{ccc|c} 1 & 0 & -31/46 & 57/46 \\ 0 & 1 & -13/46 & 15/46 \\ 0 & 0 & 1 & 1.5 \end{array} \right)$$


$$R_1 + \frac{31}{46} R_3 \rightarrow R_1 ; R_2 + \frac{13}{46} R_3 \rightarrow R_2$$

$$\left( \begin{array}{ccc|c} 1 & 0 & 0 & 2.25 \\ 0 & 1 & 0 & 0.75 \\ 0 & 0 & 1 & 1.5 \end{array} \right)$$

$$\therefore i_1 = 2.25A, i_2 = 0.75A, i_3 = 1.5A$$
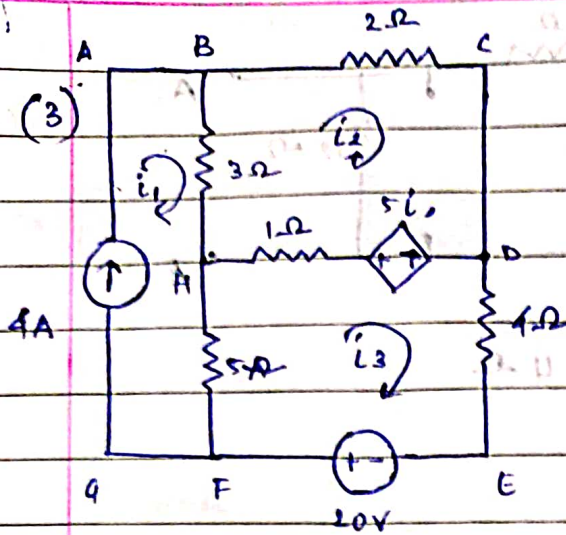
$$\text{Substituting in } I_o, I_o = 1.5A$$





$$i_o = i_o' + i_o''$$

$$\text{loop 1} \Rightarrow i_1 = 4 \text{ A}$$

BCDHB

$$\text{loop 2} \Rightarrow 2i_1 + 6i_2 - i_3 - 5i_o' = 0$$

HDEFH


$$\text{loop 3} \Rightarrow -5i_1 - i_2 + 10i_3 + 5i_o' = 0$$

$$\text{Node at H} \Rightarrow i_3 = i_1 - i_o' = 4 - i_o'$$

$$\therefore \text{loop 1 and node} \Rightarrow 3i_2 - 2i_o' = 8$$

$$\text{loop 2 and loop 3} \Rightarrow i_2 + 5i_o' = 20$$

$$i_o' = \frac{52}{17} \text{ A}$$

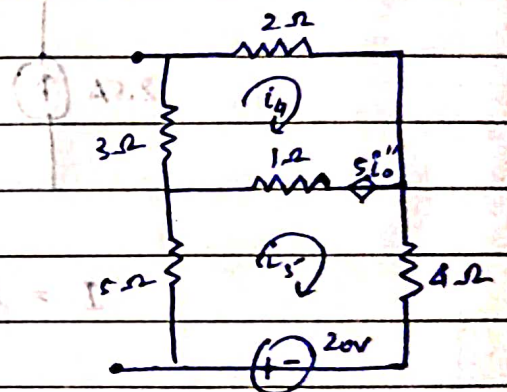

For  $i_o''$ , turn off 4A current, for the big loop, KVL  $\Rightarrow$

$$6i_4 - i_5 - 5i_o'' = 0$$

$$\text{for loop 5} \Rightarrow -i_4 + 10i_5 - 20 + 5i_o'' = 0$$

but  $i_5 = -i_o''$   $\therefore$  substituting in above eq<sup>n</sup>s  $\Rightarrow$

$$6i_4 - 4i_o'' = 0$$


$$i_4 + 5i_o'' = -20$$

solving  $\Rightarrow$

$$i_o'' = -\frac{60}{17} \text{ A}$$

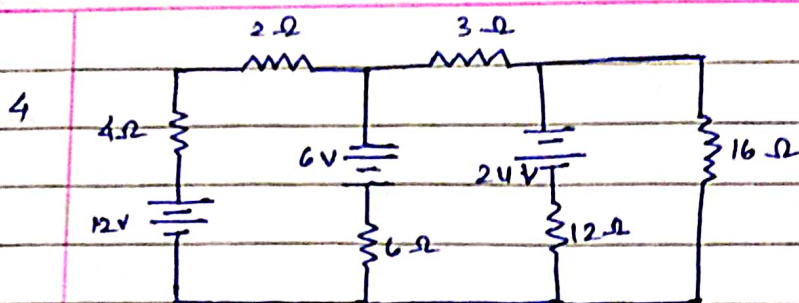
$$\text{Substituting in } i_o = i_o' + i_o'' \Rightarrow i_o = -\frac{8}{17} \text{ A}$$





Thevenin's Theorem  $\Rightarrow$

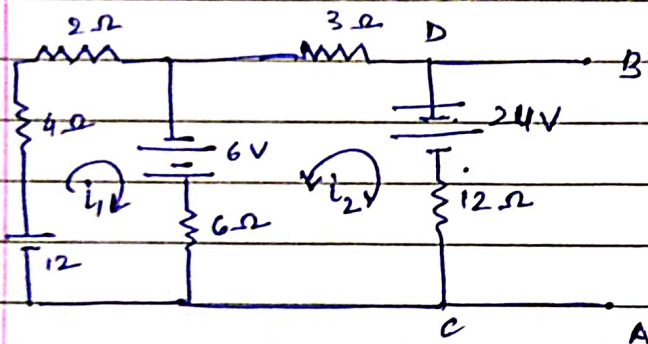remove the  $16\Omega$  resistor and find  $V$ .



KVL in loop 1

$$12 - 6I_1 + 6 - 6(I_1 + I_2) = 0$$

$$6(2I_1 + I_2) = 18$$

$$2I_1 + I_2 = 3 \rightarrow (1)$$

KVL in loop 2

$$24 - 3I_2 + 6 - (I_1 + I_2)6 - 12I_2 = 0$$

$$21I_2 + 6I_1 = 30$$

$$2I_1 + 7I_2 = 10$$

$$2I_1 + I_2 = 3 \rightarrow (2)$$

From (1) and (2),  $6I_2 = 7$  ;  $I_2 = \frac{7}{6} A$

$$\therefore I_1 = 3 - \frac{7}{6} = \frac{11}{12} A$$


$$V_{oc} = -12I_2 + 24 = -12 \times \frac{7}{6} + 24 = 10V$$

$R_{th} \Rightarrow$  4 and 2 in series = 6

6 and 6 in parallel  $\Rightarrow$  3

3 and 3 in series = 6

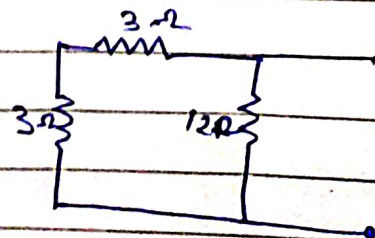6 and 12 in parallel  $\Rightarrow R_{th}$






$i$  through  $16\Omega \Rightarrow \left( R_{th} = \frac{6 \times 12}{6+12} = 4\Omega \right)$

$i = \frac{10V}{R_{th} + 16} = \frac{10}{4+16} = 0.5A$

Norton's theorem  $\Rightarrow$

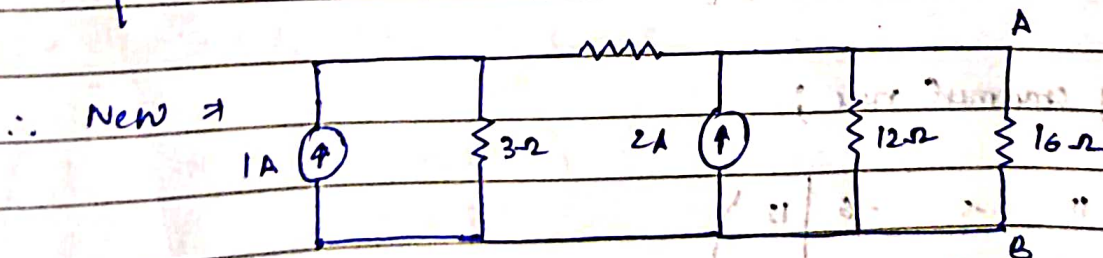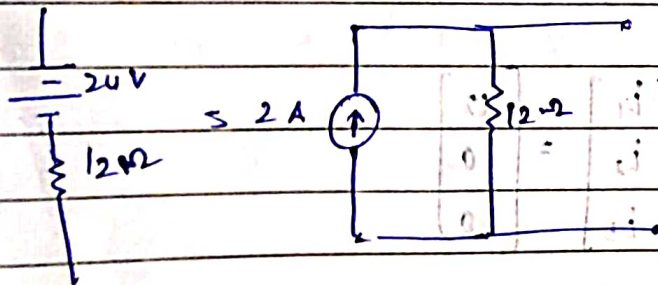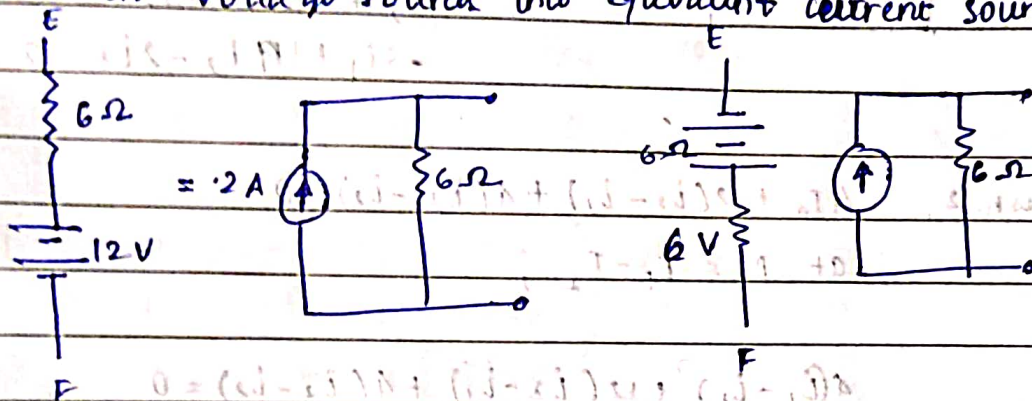Convert the voltage sources into equivalent current sources.




short A B as  $16\Omega$  is removed.

$I_{sc} = 0.5A$  for first source.

$I_{sc} = 2A$  for second source.


$\therefore I_{sc} = 0.5 + 2 = 2.5A$



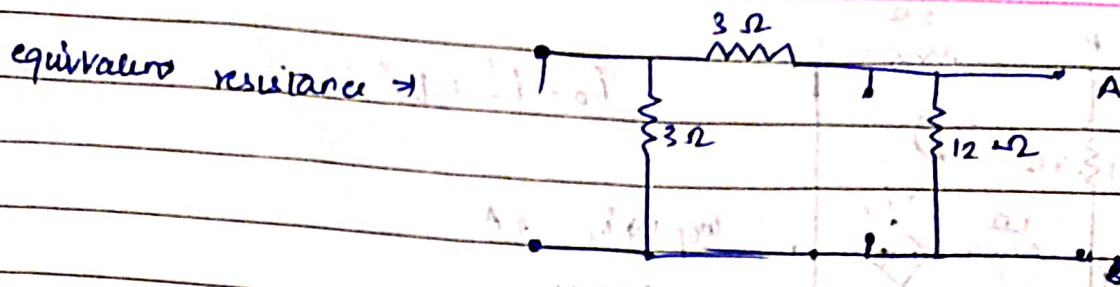

$$R_{eq} = \frac{6 \times 12}{6 + 12} = \frac{72}{18} = 4 \Omega$$

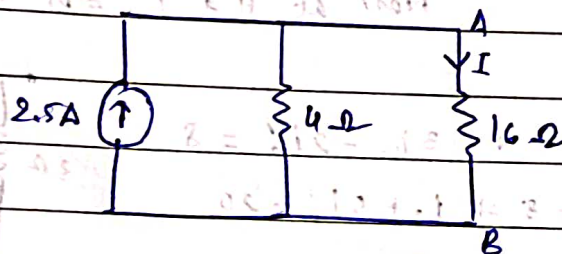$\therefore$  Norton's equivalent circuit  $\Rightarrow$



$$I = \frac{2.5 \times 4}{16 + 4} = \frac{10}{20} = \frac{1}{2} = 0.5 A$$

$\therefore$  I for both Thevenin and Norton method is same.

