

		Reg. No.:	
		Name :	




VIT[®]
BHOPAL
 www.vitbhopal.ac.in

Mid-Term Examinations – October 2021

Programme	: B.Tech (All)	Semester	: Fall 2021-22
Course	: Electric Circuits and Systems	Code	: EEE1001
Faculty	: Dr. Soumitra K Nayak	Slot/ Class No.	: E11+E12+E13/0118
Time	: 1 ½ hours	Max. Marks	: 50

Answer all the Questions

Q. No.	Sub. Sec.	Question Description	Marks
1		<p>Use nodal analysis to determine the current flowing through the various branches in the circuit as shown in Fig-1. All resistances shown are in Ohms.</p> <p>Figure - 1</p>	10
2	(a)	<p>The resistance of the various arms of a Wheatstone bridge are shown in Fig-2. The battery has an EMF of 2 V and negligible internal resistance. Using Thevenin's theorem, determine the value and direction of the current in the galvanometer circuit BD.</p> <p>Figure – 2</p>	10

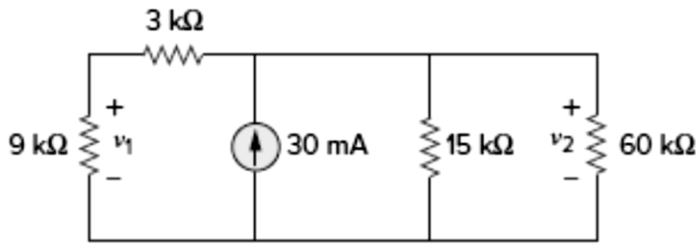3		<p>Find: (a) V_1 and V_2 as shown in Fig-3, (b) the power dissipated in the 3-kΩ and 15-kΩ resistors, and (c) the total power supplied by the current source.</p>  <p style="text-align: center;">Figure - 3</p>	10
4		<p>A half-wave rectifier circuit has been made using a step-down transformer of turn ratio 50:5. The input voltage is $v = 220\sin\omega t$ and the diode's forward resistance is 25Ω. A load resistance of 1.4 KΩ has been connected in the circuit. Assuming a secondary winding resistance of the transformer as 1.1KΩ, calculate: (a) Rms value of load current (b) rectification efficiency, and (c) ripple factor.</p>	10
5	a.	<p>Explain the operation of an enhancement type n-channel MOSFET with its characteristics graph.</p>	5
	b.	<p>In an n–p–n transistor in the common emitter configuration, an ac input signal of ± 50 mV is applied. The dc current gain, β_{dc} and ac current gain β_{ac} are 90 and 120, respectively. Calculate the voltage amplification, A_V of the amplifier. The I_B versus V_{BE} characteristic is such that for $V_B = 0.7V$, $I_B = 17mA$ and for $V_i = \pm 50mV$, $I_b = \pm 7$ mA. Also calculate the dc collector voltage.</p>	5

