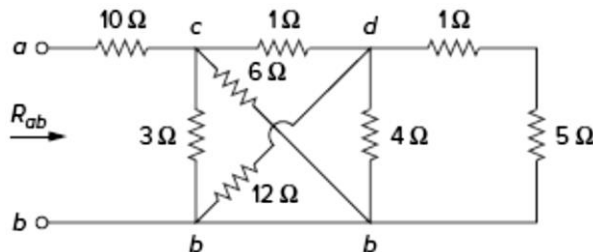


## Tutorial-1


### Electric Circuits & Systems

Date: 20.09.21


1. Find the equivalent resistance,  $R_{ab}$  for the following.



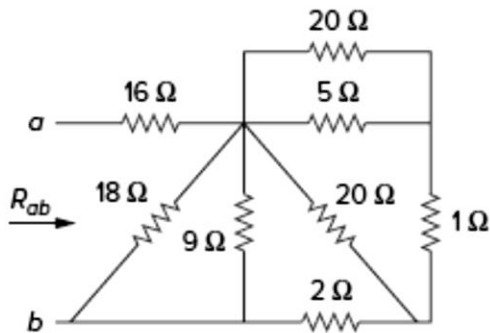2. Find the equivalent resistance,  $R_{ab}$  for the following.



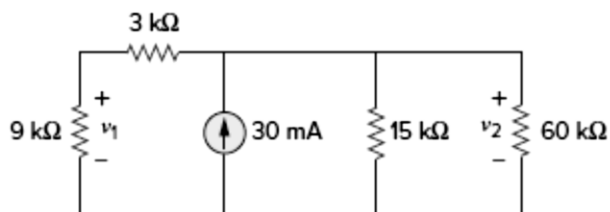3. Find: (a)  $V_1$  and  $V_2$  as shown in figure, (b) the power dissipated in the 3-k $\Omega$  and 20-k $\Omega$  resistors, and (c) the total power supplied by the current source.



4. A voltage source of  $20 \sin \pi t$  V is connected across a 5-k $\Omega$  resistor. Find the current through the resistor and the power dissipated.
5. An energy source forces a constant current of 2 A for 10 s to flow through a light bulb. If 2.3 KJ is given off in the form of light and heat energy, calculate the voltage drop across the bulb.