## **Assignment 3**

- 1) Write function of half adder. Draw and explain various implementations.
- 2) Explain about half subtractor.
- 3) What is function of binary multiplier? Explain.
- 4) Design a combinational circuit that accepts a 3-bit number and generates an output binary number equal to the square of input number.
- 5) Design a 4-bit adder subtractor circuit and explain the operation in details.
- 6) Draw and explain the working of carry look ahead adder.
- 7) Explain the functionality of a decoder.
- 8) With neat digram explain 3-8 decoder.
- 9) Implement the following Boolean function using 8:1 MUX.

$$F(A,B,C,D) = \sum (0,1,3,4,8,9,15)$$
$$F(A,B,C,D) = \sum (1,3,4,11,12,13,14,15)$$

10) Draw the basic flip-flop circuit with NAND gate and explain its operation.