

MIDSEM
EXAMINATION

NAME : Ananya Prasad

ROLLNO: 20BCE10093

SUBJECT : ECE2002

FACULTY : Dr Jitendra Kumar

SLOT : B11 + B12 + B13

SEMESTER: II

DATE : 20 April, 2021

1 Reduce the following Boolean expressions to indicated number of literals:

(i) $A'C' + ABC + AC'$ (3 literals)

$$A'C' + AC' + ABC$$

$$= C'(A' + A) + ABC$$

$$= C' \cdot 1 + ABC$$

$$= C' + ABC$$

$$= (C' + AB)(C' + C)$$

$$= AB + C'$$

=

(ii) $(x'y' + z)' + z + xy + wz$ (3 literals)

$$(x'y' + z)' + z + wz + xy$$

$$(x'y' + z') + z(1 + w) + xy$$

$$(x'y' + z') + z + xy$$

$$(x + y)z' + z + xy$$

$$(z + (x + y)) \cdot (z + z') + xy$$

$$(z + (x + y)) \cdot 1 + xy$$

$$x + y + z + xy \text{ (absorption)}$$

$$x + y + z$$

(2)


$$\begin{aligned}
 \text{(iii)} \quad & A'B(D'+C'D) + B(A+A'CD) \quad (1 \text{ literal}) \\
 &= A'BD' + A'BC'D + AB + A'BCD \\
 &= A'BD(C+C') + A'BD' + AB \\
 &= A'BD + A'BD' + AB \\
 &= A'B(D+D') + AB \\
 &= A'B + AB \\
 &= B(A'+A) \\
 &= B \\
 &=
 \end{aligned}$$

$$\begin{aligned}
 \text{(iv)} \quad & (A'+C)(A'+C')(A+B+C'D) \quad (4 \text{ literals}) \\
 & (A'+C)(A'+C')(A+B+C'D) \\
 & (A'+CC')(A+B+C'D) \\
 & A'(A+B+C'D) \\
 & AA' + A'B + A'C'D \\
 & A'B + A'C'D \\
 & A'(B+C'D) \\
 & =
 \end{aligned}$$

$$\begin{aligned}
 \text{(v)} \quad & ABC'D + A'BD + ABCD \quad (2 \text{ literals}) \\
 & ABD(C'+C) + A'BD \\
 & ABD + A'BD \\
 & BD(A'+A) \\
 & BD \\
 & =
 \end{aligned}$$


2(10)

$$x'z + w'xy' + w(x'y + y'x)$$

 

$$\Rightarrow F = xy' + wx'y + x'z$$

2(11)

 

$$F = ABC' + A'BD + B'D'$$

(iii) $A'B'C'D' + AB'D + A'BC' + ABCD + AB'C$

AB \ CD	00	01	11	10
00	1			
01	1	1		
11			1	
10		1	1	1

$$F = (A'C'D') + (AB'C) + (AB'D) + (ACD) + (A'BC')$$

(iv) $A'B'C'D' + BC'D + A'C'D + A'BCD + ACD'$

AB \ CD	00	01	10	11
00	1	1		
01		1	1	
10		1		
11				1

$$F = A'B'C' + A'BD + BC'D$$

$$=$$

3

The 3:8 line decoder is also called binary to octal decoder. There are a total of eight outputs, i.e., $Y_0, Y_1, Y_2, Y_3, Y_4, Y_5, Y_6, Y_7$ and three inputs A_0, A_1 and A_2 . This circuit has an enable E .


The main function of a decoder is to change a code into a set of signals because it is opposite to an encoder. It receives several inputs and gives decoded output.

When enable is set to 1, the truth table is as follows \Rightarrow

ENABLE	A_0	A_1	A_2	Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

When the E is low, all the output pins are low.

BLOCK DIAGRAM

 

LOGIC EXPRESSIONS:

$$Y_0 = A_0' \cdot A_1' \cdot A_2'$$

$$Y_1 = A_0 \cdot A_1' \cdot A_2'$$

$$Y_2 = A_0' \cdot A_1 \cdot A_2'$$


$$Y_3 = A_0 \cdot A_1 \cdot A_2'$$

$$Y_4 = A_0' \cdot A_1' \cdot A_2$$

$$Y_5 = A_0 \cdot A_1' \cdot A_2$$

$$Y_6 = A_0' \cdot A_1 \cdot A_2$$

$$Y_7 = A_0 \cdot A_1 \cdot A_2$$

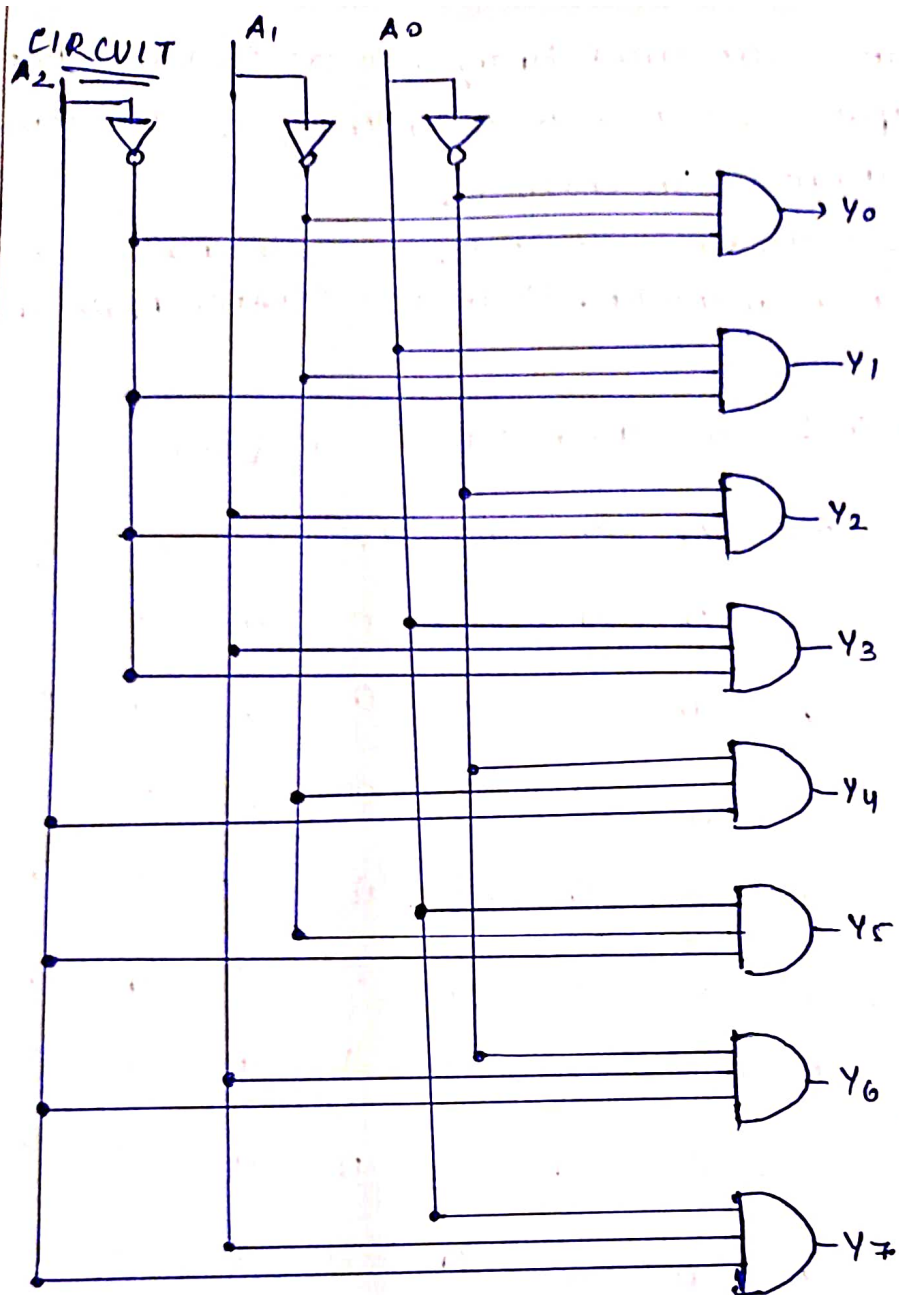


Here, there are three NOT gates and 8 three input AND gates

4 Implement the following Boolean function using 8:1 MUX.

(i) $F(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15)$


	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	1	0	\bar{A}	\bar{A}	0	0	A

 

(ii)

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$


	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	0	\bar{A}	0	1	1	A	A'	A

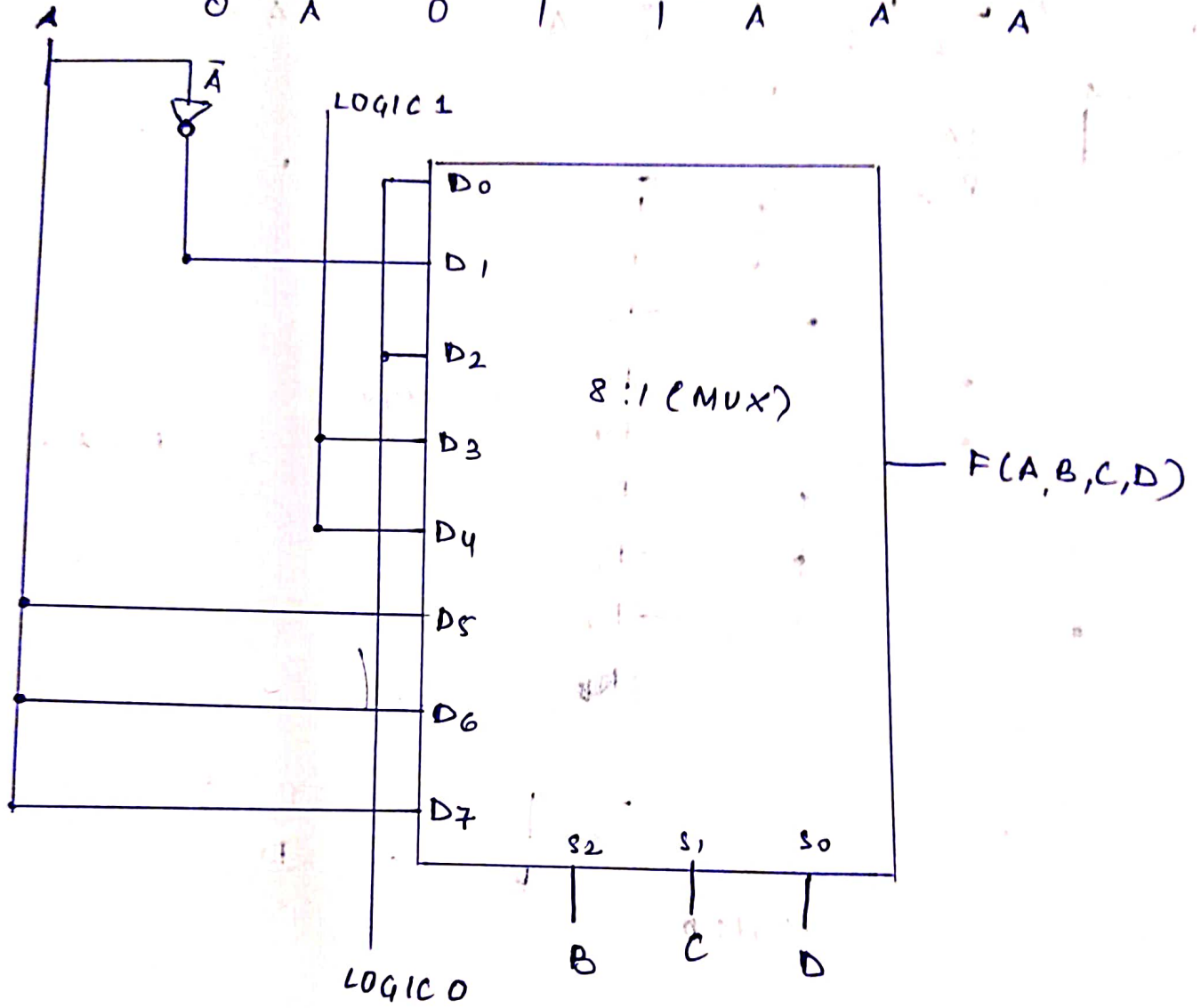

5

WORKING OF Clocked RS FLIP FLOP WITH TRUTH TABLE

- * Clock is added to an RS flip flop to control the time at which the flip flop changes the state of its output.
- * In the clocked R-S flip flop, some inputs are blocked till the receive a pulse from a source called clock. The flip flop works only when the pulse is applied according to the inputs.
- * The circuit is given by two AND gates with the regular R-S flip flop.
- * There is one more column in the table called as clock input (C).

 

CLOCKED RS FLIP FLOP

Truth table

Initial	Inputs		Output	Change shown
Q	S	R	$Q(t+1)$	
0	0	0	0	No change
0	0	1	0	Clear Q
0	1	0	1	Set Q
0	1	1	X	Indeterminate
1	0	0	1	No change
1	0	1	0	Clear Q
1	1	0	1	Set Q
1	1	1	X	Indeterminate